

Question #02:

Data:

$$C_1 = 10 \text{ MF} = 10 \times 10^{-6} \text{ F}$$

$$C_2 = 50 \text{ MF} = 50 \times 10^{-6} \text{ F}$$

$$C_3 = 25 \text{ MF} = 25 \times 10^{-6} \text{ F}$$

$$V = 250 \text{ V}$$

i) $q_1 = ?$, $q_2 = ?$, $q_3 = ?$

ii) $C_{eq} = ?$

Solution:

iii) $V_1 = ?$, $V_2 = ?$, $V_3 = ?$
Connected in series

For q_1 :-

$$q_1 = C_1 V$$

$$= 10 \times 10^{-6} \times 250$$

$$q_1 = 2.5 \times 10^{-3} \text{ C}$$

$$[q_1 = 2.5 \text{ mC}]$$

For q_2 :-

$$q_2 = C_2 V$$

$$= 50 \times 10^{-6} \times 250$$

$$q_2 = 12.5 \times 10^{-3} \text{ C}$$

$$[q_2 = 12.5 \text{ mC}]$$

For q_3 :-

$$\begin{aligned}q_3 &= CV \\&= 25 \times 10^{-6} \times 250 \\q_3 &= 6.25 \times 10^{-3} \text{ C} \\[q_3 &= 6.25 \text{ mC}]\end{aligned}$$

ii) $C_{Eq} = ?$ (Connected in parallel)

$$\begin{aligned}C_{Eq} &= C_1 + C_2 + C_3 \\C_{Eq} &= 10 + 50 + 25 \\[C_{Eq} &= 85 \mu\text{F}]\end{aligned}$$

$$\begin{aligned}Q &= CV \\V &= \frac{Q}{C}\end{aligned}$$

iii) In series

$$q = q_1 = q_2 = q_3$$

$$\therefore \frac{1}{C_{Eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_{Eq}} = \frac{1}{10} + \frac{1}{50} + \frac{1}{25}$$

$$\frac{1}{C_{Eq}} = \frac{5 + 1 + 2}{50} = \frac{8}{50}$$

$$C_{Eq} = \frac{50}{8}$$

$$[C_{eq} = 6.25 \mu F]$$

$$\therefore q = CV$$

$$q = 6.25 \times 10^{-6} \times 250$$

$$[q = 1.5625 \times 10^{-3} (= q_1 = q_2 = q_3)]$$

$$\therefore V_1 = \frac{q}{C_1}$$

$$= \frac{1.5625 \times 10^{-3}}{10 \times 10^{-6}}$$

$$[V_1 = 156.25 V]$$

$$V_2 = \frac{q}{C_2}$$

$$= \frac{1.5625 \times 10^{-3}}{10 \times 10^{-6}}$$

$$[V_2 = 31.25 V]$$

$$V_3 = \frac{q}{C_3}$$

$$= \frac{1.5625 \times 10^{-3}}{25 \times 10^{-6}}$$

$$[V_3 = 62.5]$$

Answer:

i) $q_1 = 2.5 \text{ mC}$

$q_2 = 12.5 \text{ mC}$

$q_3 = 6.25 \text{ mC}$

ii) $C_{Eq} = 85 \text{ MF}$

iii)

$V_1 = 156.25 \text{ V}$

$V_2 = 31.25 \text{ V}$

$V_3 = 62.5 \text{ V}$

Question # 03:-

Data:

$V = 100 \text{ V}$

$C_1 = 2 \text{ MF}$

$C_2 = 3 \text{ MF}$

$C_3 = 5 \text{ MF}$

$q_1 = ? , q_2 = ? , q_3 = ?$

$V_1 = ? , V_2 = ? , V_3 = ?$

Solution:

C_2 & C_3 are connected in parallel, then their equivalent C' is given as:

$$C' = C_2 + C_3 = 3 + 5 = 8 \text{ MF}$$

Now C_1 & C' are connected in series:

$$\begin{aligned}\therefore C_{Eq} &= \frac{C_1 \times C'}{C_1 + C'} \\ &= \frac{2 \times 8}{2 + 8} \\ [C_{Eq} &= 1.6 \text{ MF}]\end{aligned}$$

$$\therefore q_{Eq} = C_{Eq} V$$

$$q_{Eq} = 1.6 \times 10^{-6} \times 100$$

$$[q_{Eq} = 1.6 \times 10^{-4} \text{ C}]$$

Now C_1 & C' are in series. Both have same charge.

$$\therefore q_1 = q' = q_E = 1.6 \times 10^{-4} \text{ C}$$

$$[q_1 = 1.6 \times 10^{-4} \text{ C}]$$

$$\therefore q' = Cq'$$

$$V' = \frac{q'}{C'}$$

$$= \frac{1.6 \times 10^{-4}}{8}$$

$$[V' = 2 \times 10^{-5} \text{ V}]$$