

Chap #10 (DC-Circuits)

* Numericals (Pg #222):-

Question #01:-

Data:

Courtesy: M Ahmed Rashid BCKz

$$E_{emf} = E = 12V$$

$$r = 0.5 \Omega$$

$$I = ?$$

Solution:

For Maximum Current
load resistance = $R = 0$

$$E = I(r + R)$$

$$E = I(r + 0) \quad \therefore R = 0$$

$$E = Ir$$

$$I = \frac{E}{r}$$

$$= \frac{12}{0.5}$$

$$[I = 24 \text{ Amp}] \text{ Ans}$$

Question # 02:-

Data:

$$L = 12\text{m}$$

$$A = 4 \times 10^{-7} \text{m}^2$$

$$R = 6\Omega$$

$$\rho = ?$$

Solution:

$$R = \frac{\rho L}{A}$$

$$\rho = \frac{AR}{L}$$

$$\rho = \frac{4 \times 10^{-7} \times 6}{12}$$

$$[\rho = 2 \times 10^{-7} \Omega\text{m}] \text{Ans}$$

Question # 03:-

Data:

$$E_1 = 1.2V$$

$$l_1 = 40 \text{ cm} = 0.4 \text{ m}$$

$$l_2 = 74 \text{ cm} = 0.74 \text{ m}$$

$$E_2 = ?$$

Solution:

For balanced potentiometer:

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

$$E_2 = \frac{E_1 \times l_2}{l_1}$$

$$E_2 = \frac{1.2 \times 0.74}{0.4}$$

$$[E_2 = 2.22V] \text{ Ans}$$

Question # 04:-

Data: (Series)

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$i) R_{Eq} = ?$$

$$ii) \text{ If } V = 24V$$

$$\text{then } V_1 = ?, V_2 = ?, V_3 = ?$$

Solution:

$$\begin{aligned} R_{Eq} &= R_1 + R_2 + R_3 \\ &= 1 + 2 + 3 \\ [R_{Eq} &= 6\Omega] \end{aligned}$$

$\therefore$ First find I

$$I = \frac{V}{R}$$

$$= \frac{24}{6}$$

$$[I = 4A]$$

$$\therefore I_1 = I_2 = I_3 = I = 4A \text{ (Series)}$$

$$V_1 = I_1 R_1 = 4 \times 1 = 4V$$

$$V_2 = I_2 R_2 = 4 \times 2 = 8V$$

$$V_3 = I_3 R_3 = 4 \times 3 = 12V$$

Answer:

$$i) R_{eq} = 6\Omega$$

$$ii) V_1 = 4V$$


$$V_2 = 8V$$

$$V_3 = 12V$$

Question # 05:-

Data:

$$I = ?$$

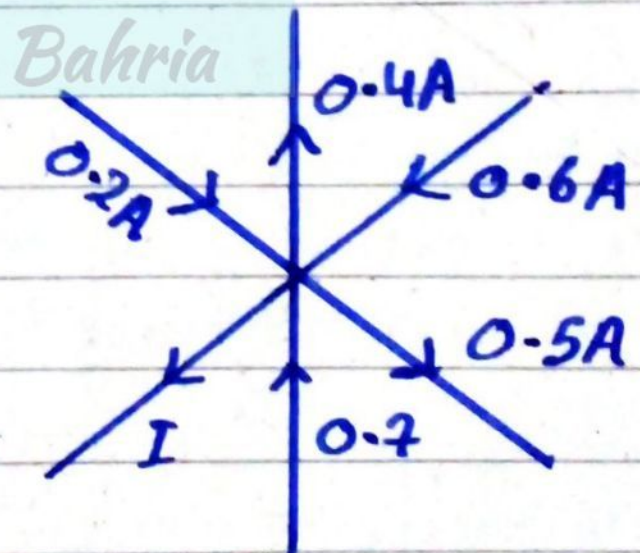

Solution:

According to Kirchhoff's law:

$$\sum I_{in} = \sum I_{out}$$

$$0.2 + 0.7 + 0.6 = I + 0.5 + 0.4$$

$$1.5 = I + 0.9$$

$$I = 1.5 - 0.9$$

$$[I = 0.6 \text{ A}] \text{ Ans}$$

Question # 06:-

Data:

$$R_1 = 15 \Omega$$

$$\frac{R_2}{n} = \frac{5}{3}$$

$$R_2 = ?$$

Solution:


$$\frac{R_2}{R_1} = \frac{l_2}{l_1}$$

$$\frac{R_2}{15} = \frac{5}{3}$$

$$R_2 = \frac{5 \times 15}{3}$$

$$[R_2 = 25 \Omega] \text{ Ans}$$

Question # 07:-

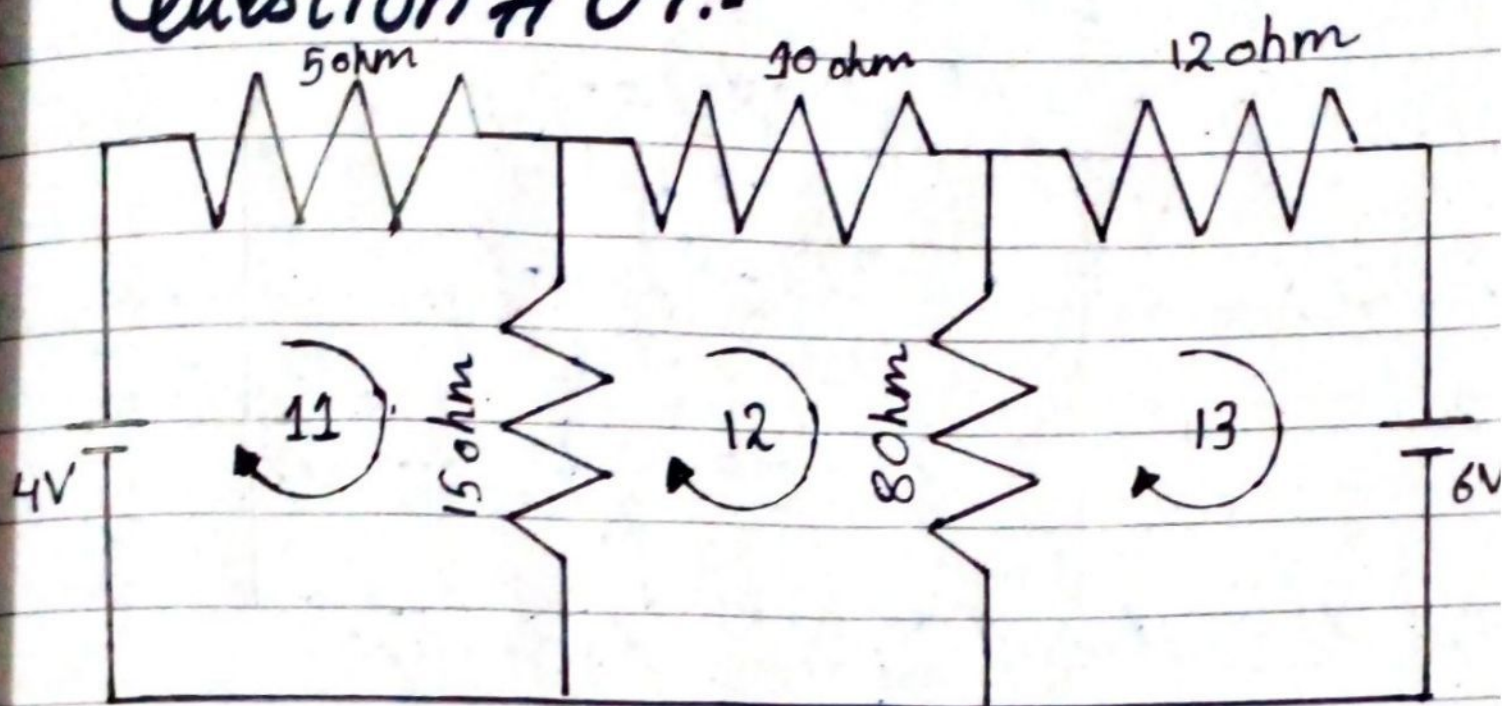

Current through 10Ω Resistance (I_2) = ?

According to Kirchhoff's law on loop # 01:-

$$5I_1 + 15(I_1 - I_2) = 4$$

$$5I_1 + 15I_1 - 15I_2 = 4$$

$$20I_1 - 15I_2 = 4$$

$$20I_1 = 4 + 15I_2$$

$$I_1 = \frac{4 + 15I_2}{20} \dots (i)$$

For loop # 02:-

$$10I_2 + 8(I_2 - I_3) + 15(I_2 - I_1) = 0$$

$$10I_2 + 8I_2 - 8I_3 + 15I_2 - 15I_1 = 0$$

$$33I_2 - 15I_1 - 8I_3 = 0 \dots (ii)$$

For loop 3:-

$$12I_3 + 8(I_3 - I_2) = -6$$

$$12I_3 + 8I_3 - 8I_2 = -6$$

$$20I_3 - 8I_2 = -6$$

$$20I_3 = -6 + 8I_2$$

$$I_3 = \frac{-6 + 8I_2}{20} \dots (iii)$$

Put the values of ' I_1 ' & ' I_3 ' in eq (ii):-

$$33I_2 - 15I_1 - 8I_3 = 0$$

$$33I_2 - 15\left(\frac{4 + 15I_2}{20}\right) - 8\left(\frac{-6 + 8I_2}{20}\right) = 0$$

$$\frac{660I_2 - 60 - 225I_2 + 48 - 64I_2}{20} = 0$$

$$660I_2 - 225I_2 - 64I_2 - 60 + 48 = 0$$

$$371I_2 - 12 = 0$$

$$371I_2 = 12$$

$$I_2 = \frac{12}{371}$$

$$[I_2 = 0.0323A \text{ (clockwise)}]$$